

Chapter 14

正弦稳态电路的频率响应

14.1 网络函数与频率响应

Network Function and Frequency Response

14.2 谐振电路的频率响应

Resonance

目标：

- a. 理解频率响应的意义，会计算电路的频率响应；
- b. 理解谐振现象及其特点，通过谐振电路的频率响应分析理解滤波的含义。

正弦稳态电路的频率响应

Q1: 下面的正弦稳态电路，参数一定，只改变电源的频率，响应如何变化？


$$\dot{U}_o(j\omega) = \frac{-j\frac{1}{\omega C}}{R - j\frac{1}{\omega C}} \times \dot{U}_s(j\omega)$$

Q2: 找出描述响应随频率变化的方法？

$$\frac{\dot{U}_o(j\omega)}{\dot{U}_s(j\omega)} = \frac{1}{1 + j\omega RC}$$

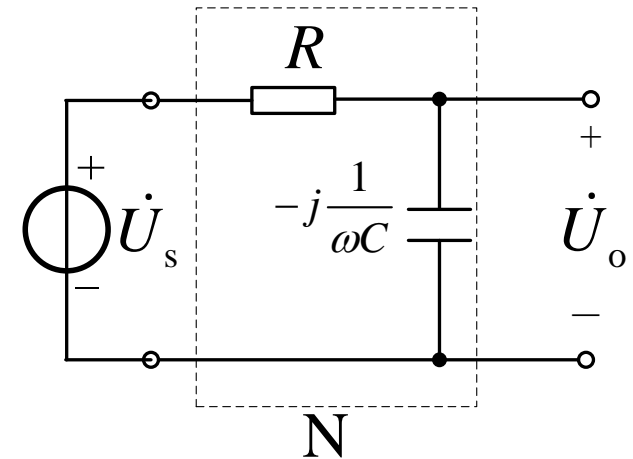Q3: 研究响应随频率变化的特点有何意义？

$$u_s = U_{dc} + \sum_k \sqrt{2}U_k \cos(k\omega t + \phi_k) \quad \longrightarrow \quad u_o = ?$$





14.1 网络函数与频率响应

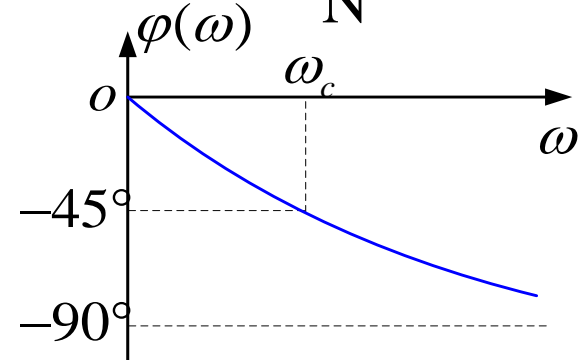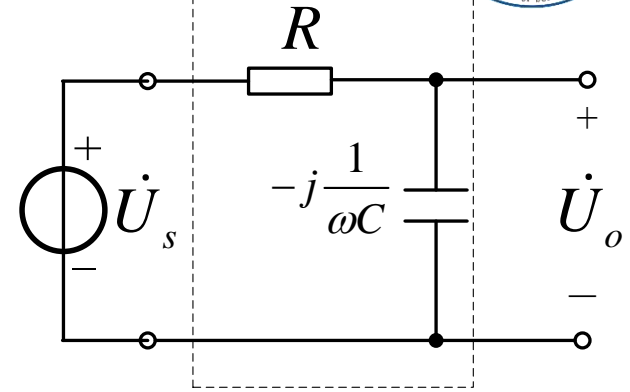1. 网络函数/传递函数

$$H(j\omega) = \frac{\text{响应}}{\text{激励}} = \frac{\dot{R}(j\omega)}{\dot{E}(j\omega)}$$

$$H(j\omega) = \frac{\dot{U}_o(j\omega)}{\dot{U}_s(j\omega)} = \frac{-j\frac{1}{\omega C}}{R - j\frac{1}{\omega C}} = \frac{1}{1 + j\omega RC}$$



2. 频率响应

频率响应：正弦稳态响应
随激励频率的变化规律。


$$H(j\omega) = |H(j\omega)| \angle \varphi(j\omega)$$

幅频响应 相频响应

$$H(j\omega) = (1 + \omega^2 R^2 C^2)^{-\frac{1}{2}} \angle -\arctan \omega RC$$

$$H(j0) = 1 \angle 0^\circ$$

$$H(j\infty) = 0 \angle -90^\circ$$

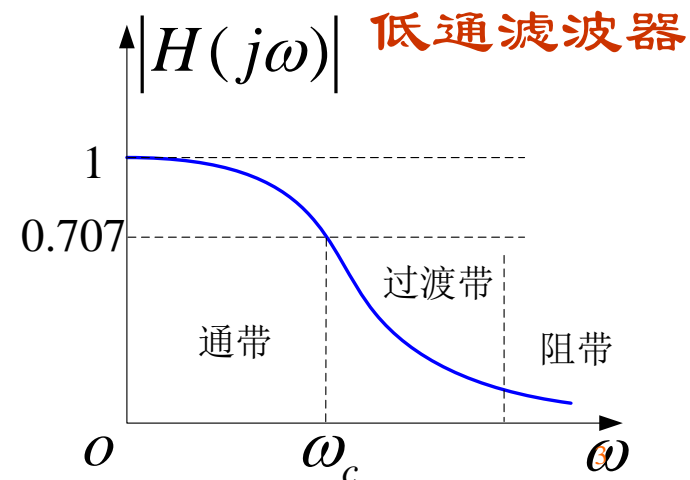

14.2 谐振电路的频率响应


1. 谐振 Resonance

$$Z_{in} = R(\omega) + jX(\omega) \quad X(\omega) = 0$$

$$Y_{in} = G(\omega) + jB(\omega) \quad B(\omega) = 0$$

\dot{U} \dot{I} 同相位，端口呈纯阻性。

$$P = UI \quad Q = 0$$

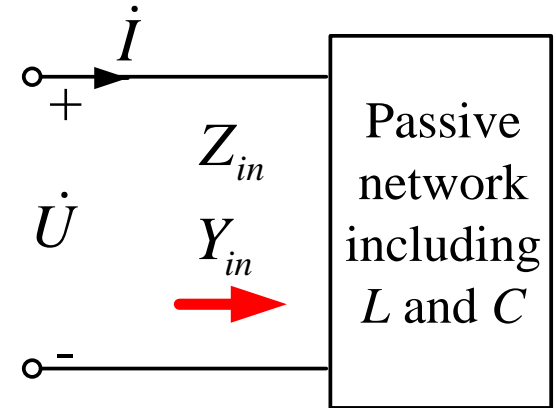


- (1) 改变激励源频率。
 - (2) 改变网络中 L 或 C 的值。
-

14.2 RLC串联谐振电路的频率响应

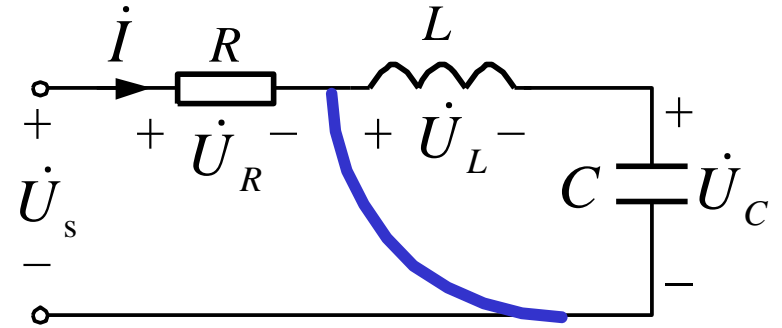2. RLC串联谐振电路及其电气特点

$$Z = R + j(\omega L - \frac{1}{\omega C})$$

$$\omega = \frac{1}{\sqrt{LC}} = \omega_0 \quad \text{谐振频率}$$



对外相当于短路！

谐振时的电气特点：

(1) \dot{U}_s and \dot{I}_0 are in phase.

(2) $|Z(\omega_0)| = R = |Z_{\min}(\omega)|$

(3) $|\dot{I}_0| = \left| \frac{\dot{U}_s}{R} \right| = |\dot{I}_{\max}(\omega)|$

(4) $\dot{U}_{R0} = \dot{U}_s$

(5) $\dot{U}_{L0} = j\omega_0 L \dot{I}_0 = j \frac{\omega_0 L}{R} \dot{U}_s$

$\dot{U}_{C0} = -j \frac{1}{\omega_0 C} \dot{I}_0 = -j \frac{1}{\omega_0 CR} \dot{U}_s$

$U_{L0} = U_{C0} = Q U_s$


Q ——品质因子

14.2 RLC串联谐振电路的频率响应

2. RLC串联谐振电路 及其电气特点

(5) 谐振下的能量关系

系统中的储能:

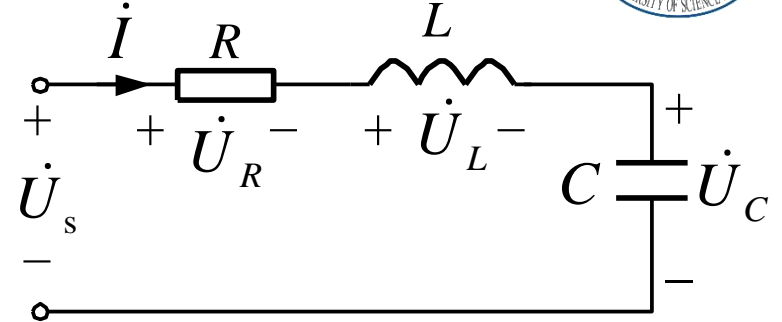

$$w_0 = w_{L0} + w_{C0} = \frac{1}{2} L i_0^2 + \frac{1}{2} C u_{C0}^2$$

$$= L I_0^2 (\cos \omega_0 t)^2 + C \left(\frac{I_0}{\omega_0 C} \right)^2 [\cos(\omega_0 t - 90^\circ)]^2$$

$$C \left(\frac{1}{\omega_0 C} \right)^2 = L \quad \xrightarrow{\text{red arrow}} \quad = L I_0^2$$

系统中的耗能(一个周期)

$$w_{R0} = \int_0^{T_0} p_{R0} dt = \int_0^{T_0} i_0^2 R dt = I_0^2 R T_0 = I_0^2 R \frac{2\pi}{\omega_0} = 2\pi I_0^2 R \sqrt{LC}$$

$$\frac{w_0}{w_{R0}} = \frac{1}{2\pi} \frac{\sqrt{L/C}}{R} = \frac{Q}{2\pi}$$

14.2 谐振电路的频率响应

3.RLC串联谐振电路的频率响应

$$|H_R(j\omega)| = \frac{|\dot{U}_R(j\omega)|}{|\dot{U}_S(j\omega)|} = \frac{R}{\left| R + j\left(\omega L - \frac{1}{\omega C}\right) \right|}$$



$$= \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R} - \frac{1}{R\omega C}\right)^2}} = \frac{1}{\sqrt{1 + Q^2\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)^2}}$$

半功率点:

$$P(\omega_{c1,c2}) = \frac{1}{2} P(\omega_0) = \frac{1}{2} \frac{U_S^2}{R} = \frac{(U_S/\sqrt{2})^2}{R}$$

$$|H_R(\eta_{c1,c2})| = \frac{1}{\sqrt{2}} = 0.707$$
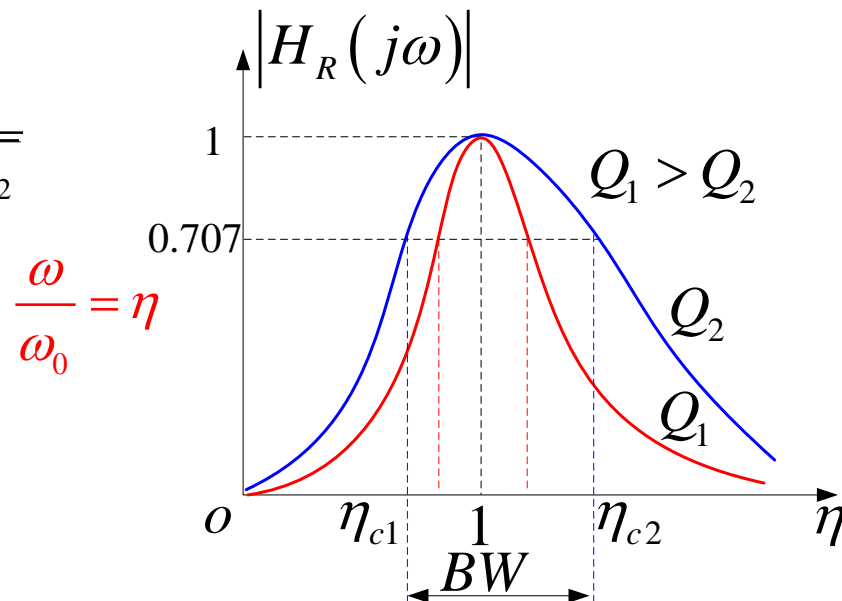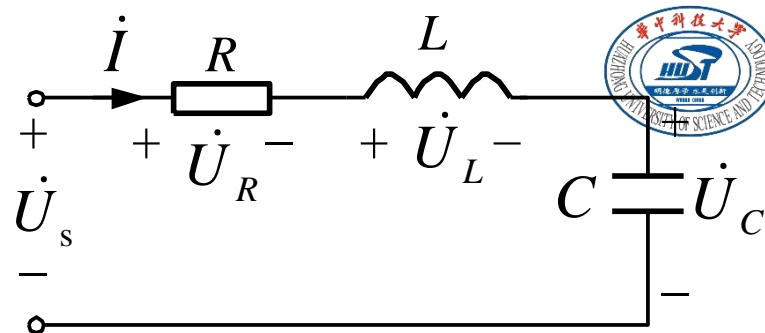
$$\left. \begin{aligned} \eta_{c1} &= -\frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \\ \eta_{c2} &= \frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \end{aligned} \right\}$$



3dB Bandwidth:

$$BW = (\eta_{c2} - \eta_{c1})\omega_0 = \frac{\omega_0}{Q}$$


$$\sqrt{\omega_{c1}\omega_{c2}} = \sqrt{\eta_{c1}\eta_{c2}}\omega_0 = \omega_0$$

$$\omega_{c1,c2} \approx \omega_0 \mp \frac{1}{2} BW \quad (\text{for } Q \geq 10)$$

14.2 谐振电路的频率响应

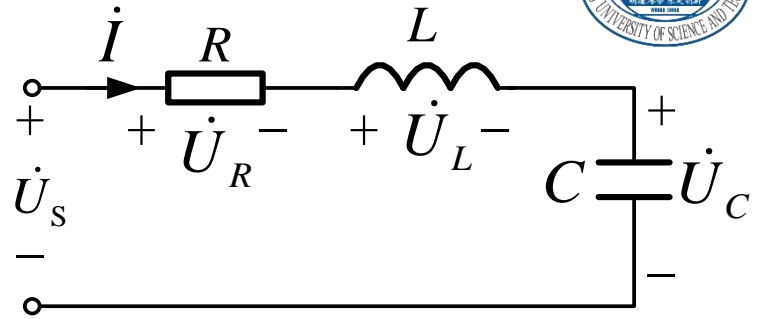3.RLC串联谐振电路的频率响应

$$\omega_0 = \frac{1}{\sqrt{LC}} = \sqrt{\omega_{c1}\omega_{c2}}$$



$$BW = \omega_{c2} - \omega_{c1} = \frac{R}{L} \quad BW = \frac{\omega_0}{Q}$$

$$Q = \frac{U_{L0}}{U_s} = \frac{U_{C0}}{U_s} \quad Q = \frac{X_{L0}}{R} = \frac{X_{C0}}{R} = \frac{\sqrt{L/C}}{R} \quad Q = 2\pi \frac{w_0}{w_{R0}} \quad Q = \frac{\omega_0}{BW}$$

$$\omega_{c1,c2} = \mp \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} = \mp \frac{\omega_0}{2Q} + \omega_0 \sqrt{1 + \left(\frac{1}{2Q}\right)^2}$$

$$\omega_{c1,c2} \approx \omega_0 \mp \frac{BW}{2} \quad (\text{For } Q \geq 10)$$

Practice

Design a series *RLC* circuit with $BW=20$ rad/s and

$\omega_0 = 1000$ rad/s. (1) Find the circuit's Q . (2) If $C=5\mu\text{F}$, find the

Value of L and R . (3) Find the cut-off frequencies.

$$BW = \frac{\omega_0}{Q} \rightarrow Q = \frac{\omega_0}{BW} = \frac{1000}{20} = 50$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 1000 \quad L = 200\text{mH}$$

$$Q = \frac{\omega_0 L}{R} \rightarrow R = \frac{\omega_0 L}{Q} = 4\Omega$$

$$\omega_{c1,c2} \approx \omega_0 \mp \frac{BW}{2} = 990\text{rad/s}, 1010\text{rad/s}$$

14.2 谐振电路的频率响应

4.RLC并联谐振电路

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\bullet \dot{I}_{R0} = \dot{I}_S$$

$$\bullet \dot{U}_0 \text{ and } \dot{I}_S \text{ are in phase.}$$


$$\bullet |Y(\omega_0)| = G = |Y_{\min}(\omega)|$$

$$\bullet |\dot{U}_0| = \left| \frac{\dot{I}_S}{G} \right| = |\dot{U}_{\max}(\omega)|$$

$$\bullet \dot{I}_{L0} = \frac{\dot{U}_0}{j\omega_0 L} = -j \frac{R}{\omega_0 L} \dot{I}_S$$

$$\bullet \dot{I}_{C0} = j\omega_0 C \dot{U}_0 = j \omega_0 C R \dot{I}_S$$

$$\bullet I_{L0} = I_{C0} = Q I_S$$

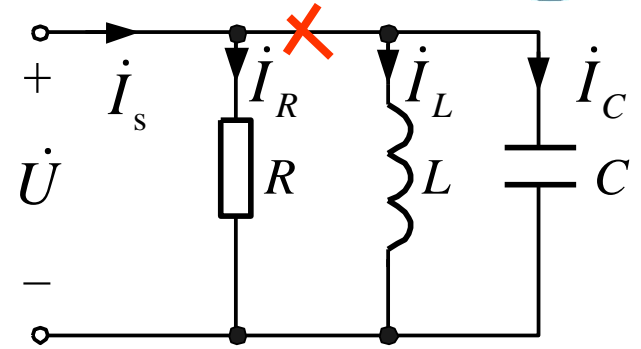

$$\omega_{c1,c2} = \mp \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$BW = \frac{1}{RC}$$

$$\left. \begin{array}{l} R \rightarrow G \\ L \rightarrow C \\ C \rightarrow L \\ \dot{U} \rightarrow \dot{I} \\ \dot{I} \rightarrow \dot{U} \end{array} \right\} \begin{array}{l} \text{串联} \\ \text{并联} \end{array}$$

14.2 谐振电路的频率响应

5. 其他谐振电路

与串联或并联谐振电路等效!

$$Y = \frac{1}{R_1 + j\omega L_1} + j\omega C_2$$



$$= \frac{R_1}{R_1^2 + (\omega L_1)^2} + j[\omega C_2 - \frac{\omega L_1}{R_1^2 + (\omega L_1)^2}]$$

$$= G + j(\omega C - \frac{1}{\omega L})$$

$$\omega_0 C_2 = \frac{\omega_0 L_1}{R_1^2 + (\omega_0 L_1)^2}$$


$$\omega_0 = \frac{1}{\sqrt{L_1 C_2}} \sqrt{1 - \frac{C_2 R_1^2}{L_1}} \quad (L_1 > C_2 R_1^2)$$
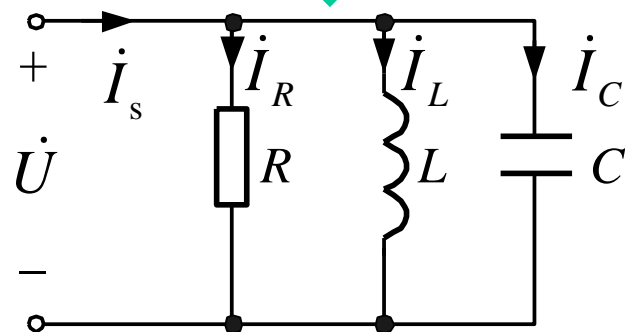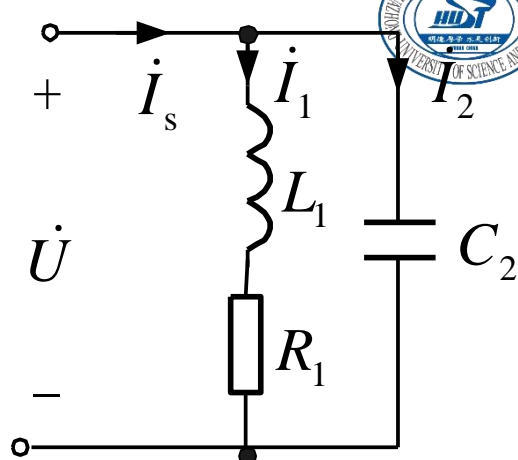
$$Q = \frac{B_{L0}}{G} = \frac{\omega_0 L_1}{R_1} = \sqrt{\frac{L_1}{C_2 R_1^2} - 1}$$



$$I_{20} = Q I_s$$
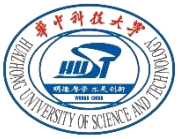
$$I_{10} = \sqrt{I_s^2 + (Q I_s)^2} = I_s \sqrt{1 + Q^2}$$



作业

- 14.3 节：14-9, 14-10
- 14.4 节：14-14